

# Electronic Circuits

## Final Exam Spring 2020

Q1.

(Marks: 10)

For the network of Fig. 1, determine the following:

- a) Voltage  $V_C$  across the capacitor
- b) Draw the output waveform

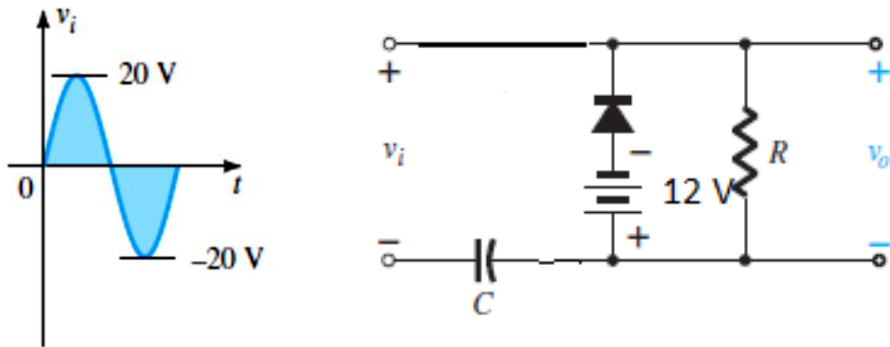


Figure 1

Q2.

(Marks: 10)

For the network of Fig. 2, determine:

- a.  $I_E$ .
- b.  $V_C$ .
- c.  $V_{CE}$ .

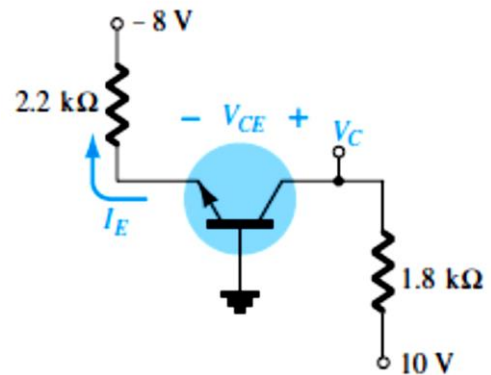


Figure 2

Q3.

(Marks: 10)

For the common-base configuration of Fig. 3:

- Determine  $r_e$ .
- Find  $Z_i$  and  $Z_o$ .
- Calculate  $A_v$ .

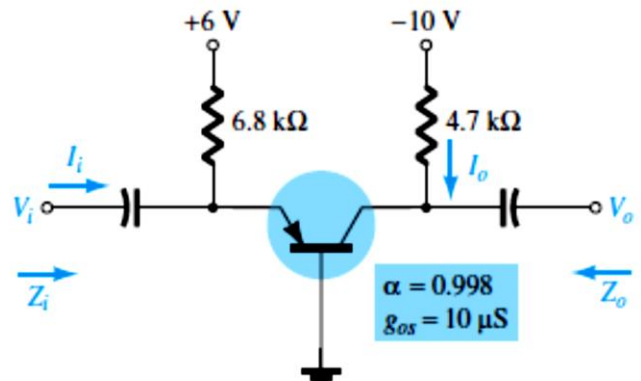


Figure 3

Q4.

(Marks: 10)

- Given  $I_{DSS} = 12$  mA and  $V_P = -4$  V, sketch the transfer characteristics for the JFET transistor using shorthand method.
- Sketch the drain characteristics for the device of part (a).

Q5.

(Marks: 10)

Sketch the schematic diagram of a CMOS inverter. If the supply voltage is 5V, and  $V_{in} = 0$  V, determine the exact value of output voltage for the following values of currents and voltages of MOSFET:

"ON" MOSFET:  $I_D = 4$  mA,  $V_{DS} = 0.1$  V.

"OFF" MOSFET:  $I_D = 0.5$  μA.

Q6.

(Marks: 10)

For the network of Fig. 4, determine:

- $V_G$ .
- $I_{DQ}$  and  $V_{GSQ}$ .
- $V_D$  and  $V_S$ .
- $V_{DSQ}$ .

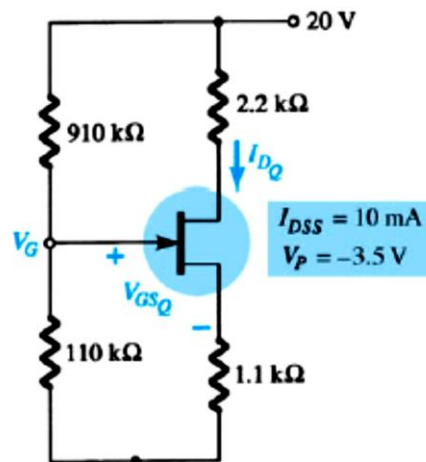


Figure 4

END